

Lab 4 – Combinational Circuits

CS1050 Computer Organization and Digital Design

Dept. of Computer Science and Engineering, University of Moratuwa

Learning Outcomes

In this lab we will design a decoder and a multiplexer. Decoders and multiplexers are 2 of the key components of a microprocessor. After completing the lab, you will be able to:

- Design and develop a 3-to-8 decoder
- Design and develop a 8-to-1 multiplexer
- Verify their functionality via simulation and on the development board


Introduction

A decoder converts binary data from n coded inputs to a maximum of 2^n unique outputs. The decoder that we are going to build also has an enable pin/input. Enable input must be on for the decoder to function, otherwise we assume its outputs as a “disabled” output. A multiplexer receives binary data from 2^n lines and connect them to a single output line based on a given nbit selection. We will also add an enable pin to the multiplexer.

Decoders and multiplexers are 2 key components of a microprocessor. We will later use these components to build our simple microprocessor.

Building the Circuits

 We will first build a 2-to-4 decoder as shown in Fig 1. Then by combining two 2-to-4 decoders we will build a 3-to-8 decoder. Then finally using 3-to-8 decoder we will build 8_to_1_multiplexer.



Source: <http://users.cis.fiu.edu/~prabakar/cda4101/Common/notes/lecture08.html>

Figure 1 – 2-to-4 decoder.

- Step 1:
- Building a 2-to-4 decoder vhdl file.
 - Name the project as Lab 4 and the design file as **Decoder_2_to_4**.

Step 2: Using busses.

Instead of defining separate labels for each input and output as I0, I1, Y0, Y1, Y2, and Y3 we can define these as busses.

In digital design a bus is a collection of wires that carry data across multiple entities/modules. Then each wire in the bus can be separately accessed based on a zero-based index (like accessing an array variable).

When defining the module define the inputs and outputs as I, EN, and Y as seen in Fig. 2. Click Ok.

Define a module and specify I/O Ports to add to your source file.
For each port specified:
MSB and LSB values will be ignored unless its Bus column is checked.
Ports with blank names will not be written.

Module Definition

Entity name:

Architecture name:

I/O Port Definitions

Port Name	Direction	Bus	MSB	LSB
I	in	<input checked="" type="checkbox"/>	1	0
EN	in	<input type="checkbox"/>	0	0
Y	out	<input checked="" type="checkbox"/>	3	0

OK Cancel

Figure 2 – Defining inputs and outputs as busses for Decoder_2_to_4.

You would see the following lines added to your VHDL file:

```
entity Decoder_2_to_4 is
  Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (3 downto 0));
end Decoder_2_to_4;
```

The `std_logic_vector` VHDL type is used to define arrays of `std_logic` variables. Here `3 downto 0` indicates that the bus has four wires labelled from bit 3 (MSB) to 0 (LSB).

Step 3: Simulating circuit.

Simulate the circuit using XSim and make sure your decoder functions correctly. Name the Test Bench File as **TB_Decoder_2_to_4**.

Step 4: Build a 3-to-8 decoder.

Create a new design file and save it as **Decoder_3_to_8**. Label inputs and outputs as **I**, **EN**, and **Y**. Make **I** as a 3-bit bus while **Y** as a 8-bit bus. Using two 2-to-4 decoders (label as **Decoder_2_to_4_0** and **Decoder_2_to_4_1**) and other gates, build a 3-to-8 decoder. You need to use the component keyword to add decoders.

Your final VHDL code could look like the following:

```
entity Decode_3_to_8 is
  Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decode_3_to_8;
architecture Behavioral of Decode_3_to_8 is
  component Decode_2_to_4
    port(
      I: in STD_LOGIC_VECTOR;
      EN: in STD_LOGIC;
      Y: out STD_LOGIC_VECTOR );
  end component;
  signal I0,I1 : STD_LOGIC_VECTOR (1 downto 0);
  signal Y0,Y1 : STD_LOGIC_VECTOR (3 downto 0);
  signal en0,en1, I2 : STD_LOGIC;
begin
  Decode_2_to_4_0 : Decode_2_to_4
    port map(
      I => I0,
      EN => en0,
      Y => Y0 );
  Decode_2_to_4_1 : Decode_2_to_4
    port map(
      I => I1,
      EN => en1,
      Y => Y1 );
  en0 <= NOT(I(2)) AND EN;
  en1 <= I(2) AND EN;
  I0 <= I(1 downto 0);
  I1 <= I(1 downto 0);
  I2 <= I(2);
  Y(3 downto 0) <= Y0;
  Y(7 downto 4) <= Y1;
end Behavioral;
```

If **Decoder_3_to_8** is not automatically set as the top-level design set it.

Simulate the new decoder using XSim and make sure it functions correctly. Name the Test Bench File as **TB_Decoder_3_to_8**. It is not essential to try all the possible combinations of inputs. Instead, you can try a subset of the possible inputs.

Here is a method to try several input combinations based on your index number (this also enables your instructor to make sure each student uses a unique simulation pattern). Consider the 6 digits of your index number. Then convert your index number to binary. Set **I(2)** to **I(0)** according to the 3 Least Significant Bits (LSBs) of your index number. Then try the next 3 LSBs, and so on. For example, suppose your index number is 123456R. Then its binary representation is 011 110 001 001 000 000 (ignoring the check digit). Try setting **I(2) – I(0)** as 000, then 001, 110, and so on. You may ignore repetitive values.

Step 5: Designing an 8-to-1 multiplexer.

Take a piece of paper and draw a logic circuit of an 8-to-1 multiplexer built using 3-to-8 decoder. You may also need several AND and OR gates. Label your input and output pins as **S**, **D**, **EN**, and **Y** (**Y** is the output). Both **S** and **D** should be buses of appropriate size.

Name the design file as **Mux_8_to_1**. Build the circuit and simulate the multiplexer.

Similar to Step 4 try a set of input combinations based on your index number. Make sure your multiplexer is functioning correctly.

Step 6: Connecting inputs and outputs.

Input and output pins are connected only to the top-level design. Therefore, first make sure multiplexer is already set as the Top Design. Connect switches **SW0** to **SW7** as the inputs (from **D0** to **D7**) to **Mux_8_to_1**.

Connect push button **BTN0** to **EN**. Connect **SW13** to **SW15** to control pins **S0** to **S2**. Set output **Y** to LED **LD0**.

Step 7: Test on BASYS 3.

Generate the programming file (i.e., bitstream) and load it to the BASYS 3 board. Change the switches and push buttons on the board and verify the functionality of your multiplexer (check the output on LED).

Step 10: Lab Report.

You need to submit a report for this lab. Your report should include the following:

- Student name and index number. Do not attach a separate front page
- State the assigned lab task in a few sentences
- All VHDL codes
- RTL Analysis elaborated design schematics
- All timing diagrams. Show all possible inputs for 2-to-4 decoder. For 3-to-8 decoder and 8-to-1 multiplexer use your index number as the input
- Conclusions from the lab

Submit the lab report at the beginning of the next lab.

Prepared By

- Dilum Bandara, PhD – Feb 19, 2014.
- Updated on Oct 03, 2018.
- Updated by Chathuranga Hettiarachchi, PhD – May 31, 2022.